

>> Name of Mini Project :

Simple Digital Voltmeter Circuit with PCB
using ICL7107

>> Block Diagram :

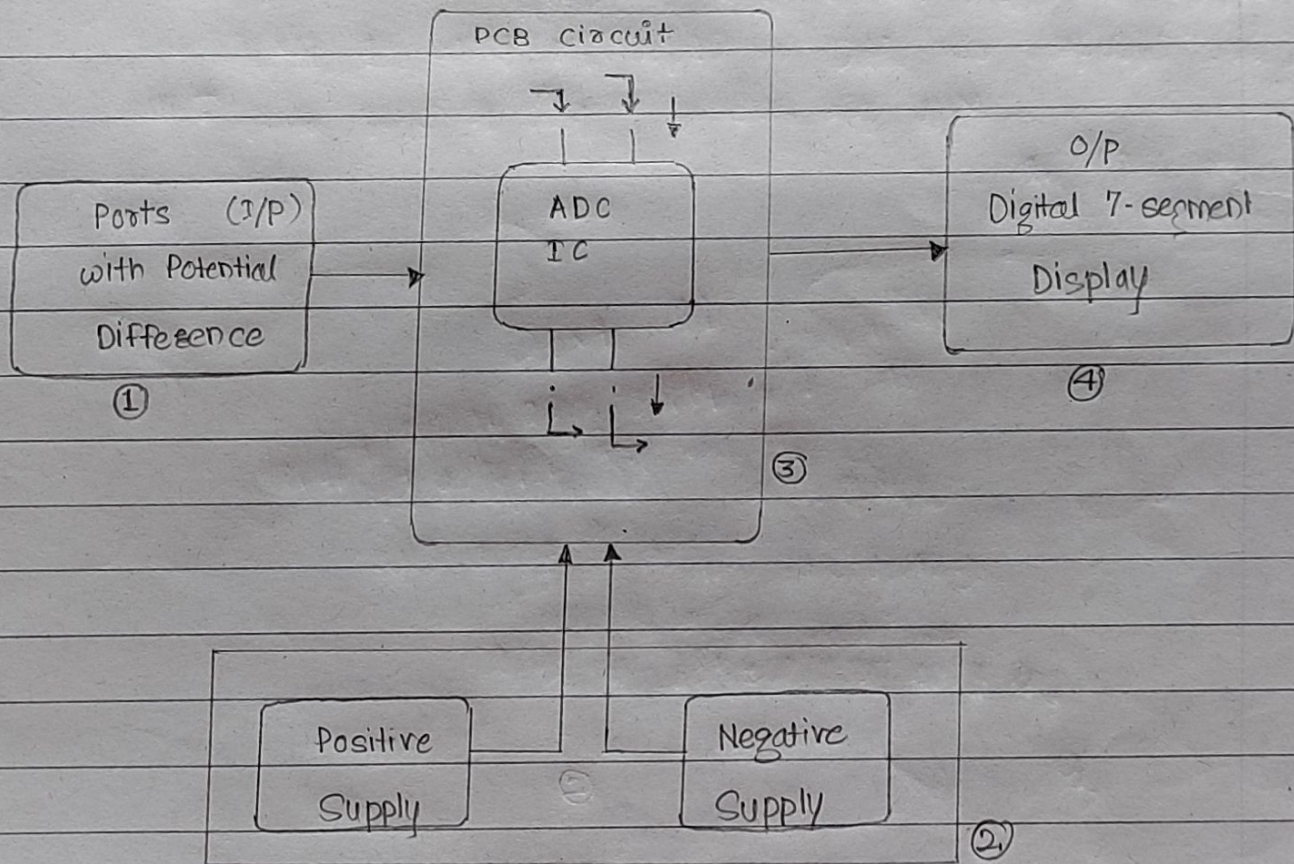


Fig: Block Diagram Representation of Simple Digital Voltmeter circuit with PCB using ICL7107

Functional Characteristics

Block 1 : [I/p] Ports with Potential Difference

- The block represents the i/p of the circuit testing
- It comprises of two ports having potential difference with respect to each other.

(Note: The maximum value of Potential Difference should not go beyond scope of the circuit capacity.)

Block 2 : Positive and Negative Supply

- Power supply is necessary for the circuit operation.
- Two supplies (one with '+ve terminal & another with '-ve') are given the Digital Voltmeter circuit.

Block 3 : PCB Circuit

- The PCB circuit is the main body of the project.
- It comprises of all the circuit elements connected in proper manner
- It follows a series of processes to get the Potential Difference between the i/p ports in the Analog form.

➤ Functional Characteristics

Simple Digital Voltmeter Circuit

Block 1 : [I/p] Ports with Potential Difference

- The block represents the i/p of the circuit testing
- It comprises of two ports having potential difference with respect to each other.

(Note: The maximum value of Potential Difference should not go beyond scope of the circuit capacity.)

Block 2 : Positive and Negative Supply

- Power supply is necessary for the circuit operation.
- Two supplies (one with '+ve terminal & another with '-ve') are given the Digital Voltmeter circuit.

Block 3 : PCB Circuit

- The PCB circuit is the main body of the project.
- It comprises of all the circuit elements connected in proper manner
- It follows a series of processes to get the Potential Difference between the i/p ports in the Analog form.

Function : This analog potential difference so obtained is converted into digital form by using Analogue-to-Digital Converter IC.

Block 1 : The Digital value of potential difference so obtained is the required O/P from the PCB circuit.



Block 4 : [O/P] Digital Display

- The digital value of potential difference obtained at the end of Block 3 functionality is sent to the digital display.

- The digital 7-segment display is capable of showing the closest-almost value of potential difference between the two ports taken as input in Block 1.

Block 5 : PCB Circuit

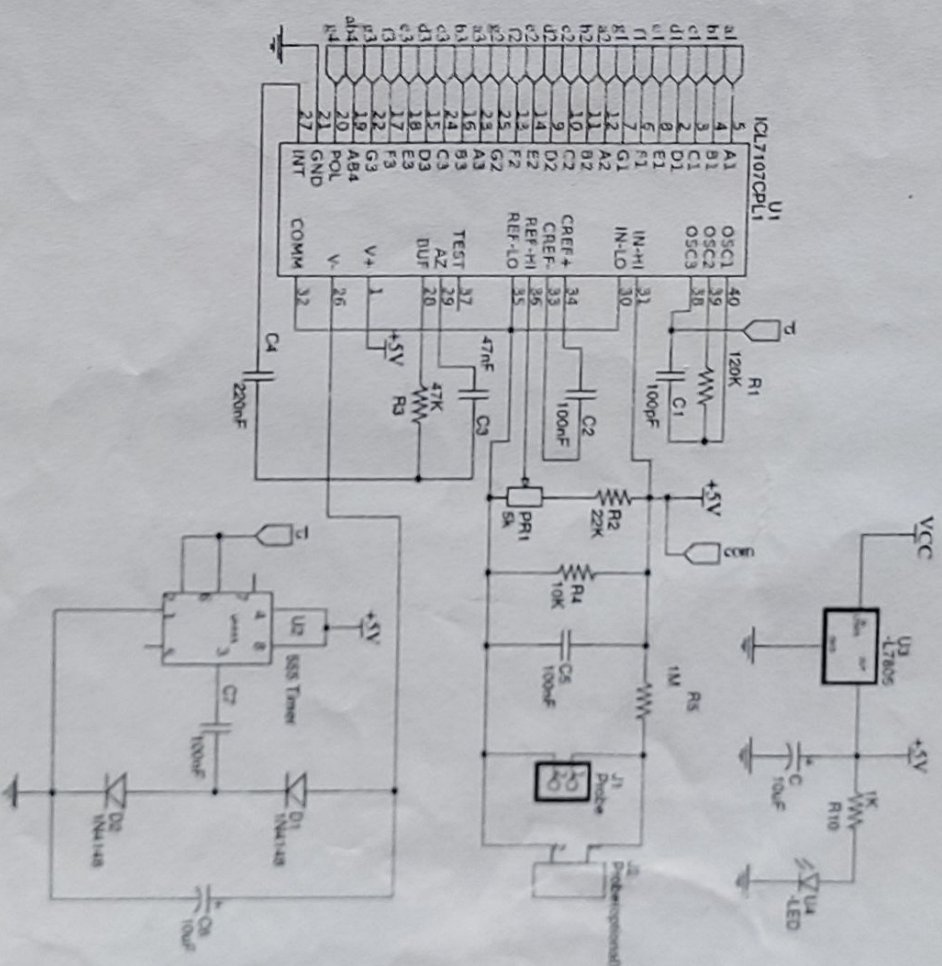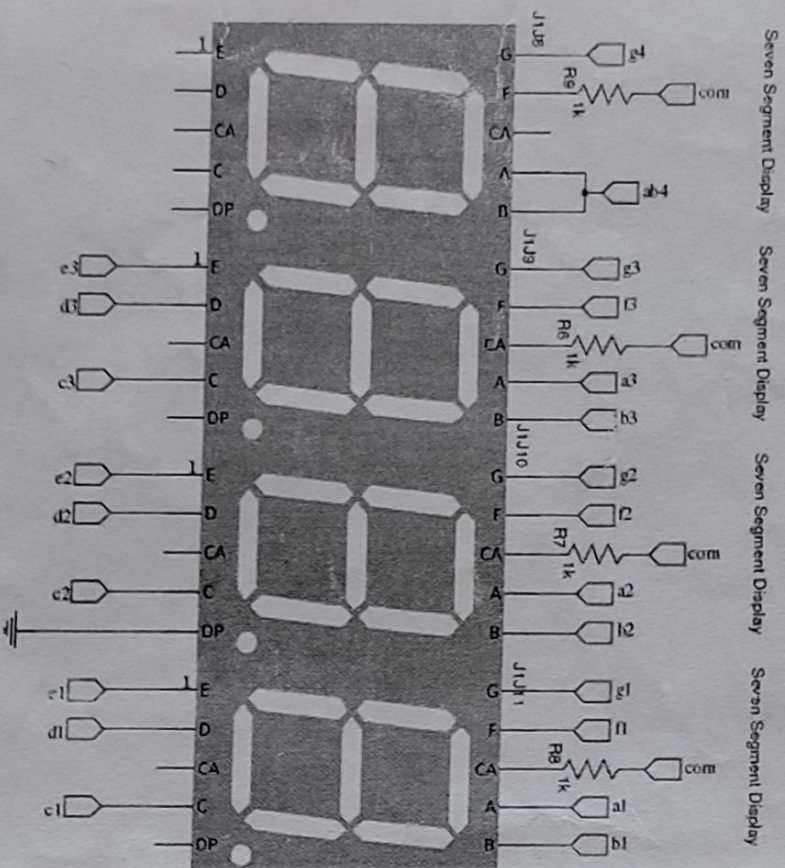EDW/MP : Simple Digital Voltmeter : Circuit Diagram



TITLE:		REV:
Date:		Sheet:
EasyEDA V4.1.3		Drawn By:

